

Circuits & 2-adic Integers

Jean Vuillemin

École Normale Supérieure de Paris

Digital Synchronous Circuit



2-adic Integers

Arithmetic Circuits

LHC Application


Synchronous Binary Signals

EBM Images @1GHz

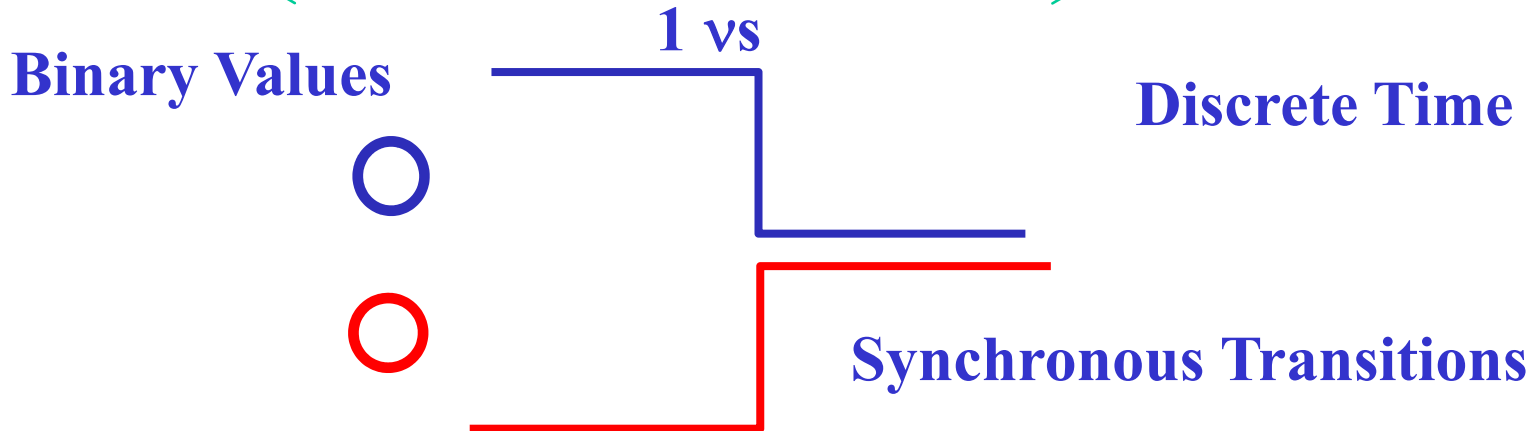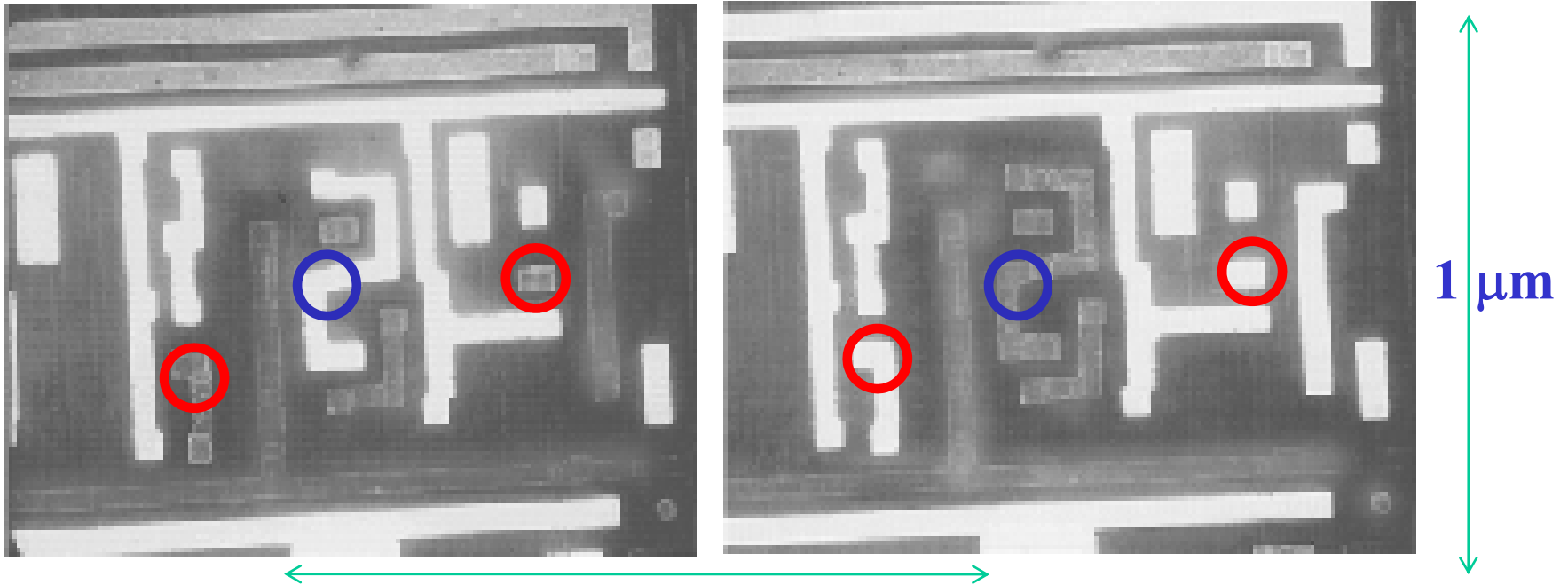


Synchronous *Gates*

Boolean Gates

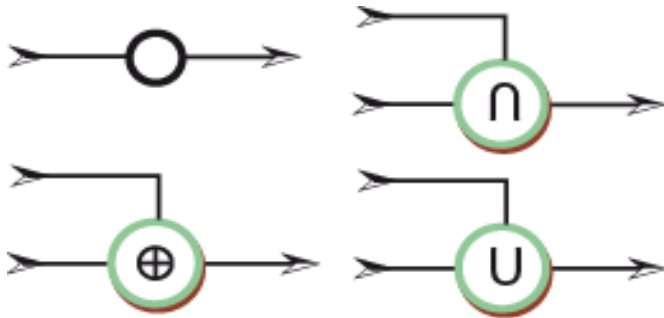

Register

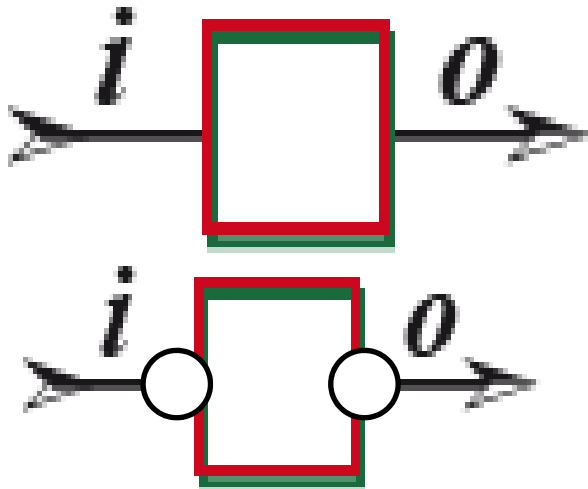

$$\neg a_t = 1 - a_t$$

$$a_t \oplus b_t = a_t + b_t - 2a_t b_t$$

$$a_t \cup b_t = a_t + b_t - a_t b_t$$

$$a_t \cap b_t = a_t b_t$$



$$o_0 = 0, o_{t+1} = i_t$$

$$o_0 = 1, o_{t+1} = i_t$$

Half Adder

$$\text{halfAdd}(a, b, c) = (s, r)$$
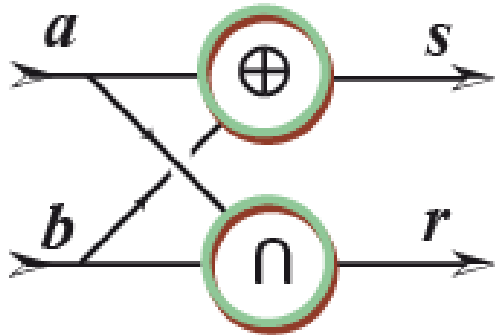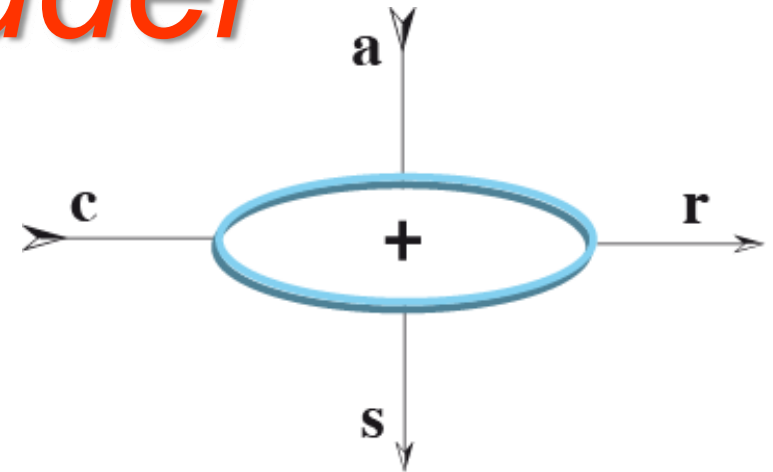
$$\left\{ \begin{array}{l} s = a \oplus b \\ r = a \cap b \end{array} \right\}$$



$$s_t = a_t \oplus b_t = a_t + b_t - 2a_t b_t$$

$$r_t = a_t \cap b_t = a_t b_t$$

$$\forall t : a_t + b_t = s_t + 2r_t$$

Digital Synchronous Circuit

- Syntax
 - Compose *In, And, Xor, Reg*
 - Feed-forward Boolean Gates & Clocked feed-back
 - Hierarchical Netlist
- Semantics
 - All variables have binary values at all times
 - Zero delay: *Not, And, Xor* Unit delay: *Reg*
 - All transitions happen at clock signal
- Global clock
 - Isochronous distribution through entire chip
 - Clock period can be constant or variable
 - Clock period exceeds all transition delays

Binary Integers

n	B_0^n	B_1^n	B_2^n	B_3^n	$B_{k>3}^n$	$\{k \in n\}$
0	0	0	0	0	0	$\{\}$
1	1	0	0	0	0	$\{0\}$
2	0	1	0	0	0	$\{1\}$
3	1	1	0	0	0	$\{0, 1\}$
4	0	0	1	0	0	$\{2\}$
5	1	0	1	0	0	$\{0, 2\}$
6	0	1	1	0	0	$\{1, 2\}$
7	1	1	1	0	0	$\{0, 1, 2\}$
8	0	0	0	1	0	$\{3\}$

n	B_0^n	B_1^n	B_2^n	B_3^n	$B_{k>3}^n$	$\{k \in n\}$
-1	1	1	1	1	1	$\neg\{\}$
-2	0	1	1	1	1	$\neg\{0\}$
-3	1	0	1	1	1	$\neg\{1\}$
-4	0	0	1	1	1	$\neg\{0, 1\}$
-5	1	1	0	1	1	$\neg\{2\}$
-6	0	1	0	1	1	$\neg\{0, 2\}$
-7	1	0	0	1	1	$\neg\{1, 2\}$
-8	0	0	0	1	1	$\neg\{0, 1, 2\}$
-9	1	1	1	0	1	$\neg\{3\}$

$$n = \sum_k B_k^n 2^k = \sum_{k \in n} 2^k$$

$$\neg 0 = 1 + 2 + 4 + 8 + 16 + \dots = -1$$

$$k \in n \Leftrightarrow 1 = B_k^n$$

$$\neg n = -(n + 1)$$

2-adic Addition

	<i>a</i>	1	1	1	0	1	0	...
+	<i>b</i>	1	0	1	1	1	0	...
<hr/>								
	<i>c</i>	0	1	1	1	1	1	...
	<i>s</i>	0	0	1	0	1	1	

$$a_t + b_t + c_t = s_t + 2c_{t+1}$$

Magic Masks

k	B_k^{-1}	B_k^{-2}	B_k^{-3}	B_k^{-4}	B_k^{-5}	...	μ_k
0	1	0	1	0	1	...	-1/3
1	1	1	0	0	1	...	-1/5
2	1	1	1	1	0	...	-1/17

$$\mu_k = \sum_n B_k^{-n} 2^n = \sum_{n \notin k} 2^n$$

$$\mu_k = (1^{2^k} 0^{2^k})^\infty = \frac{-1}{1 + 2^{2^k}}$$

$$\mu_0 : 10101010\dots$$


$$3\mu_0 = -1$$

$$+2\mu_0 : 01010101\dots$$

$$= 3\mu_0 : 11111111\dots$$

$$\mu_0 = 1 + 4 + 16 + \dots = -\frac{1}{3}$$

2-adic Gates

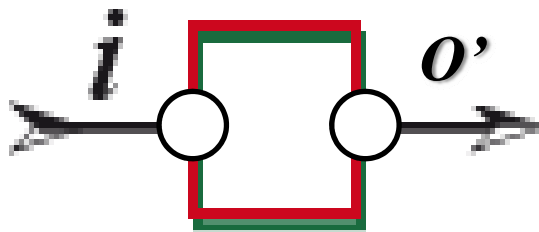


$$o_0 = 0, \quad o_{t+1} = i_t$$

$$o = \sum o_t 2^t \quad i = \sum i_t 2^t$$

$$o = 2i$$

$$o' = 1 + 2i$$

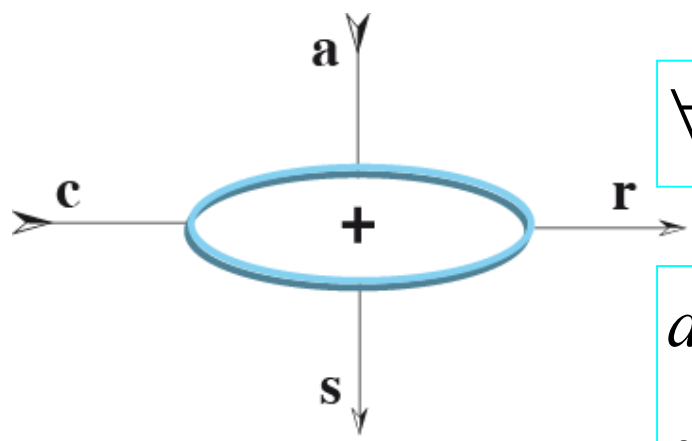

$$\forall t: a_t + b_t = s_t + 2r_t$$



$$a = \sum a_t 2^t \quad b = \sum b_t 2^t$$

$$s = \sum s_t 2^t \quad r = \sum r_t 2^t$$

$$a + b =$$

$$s + 2r$$

Serial Increment

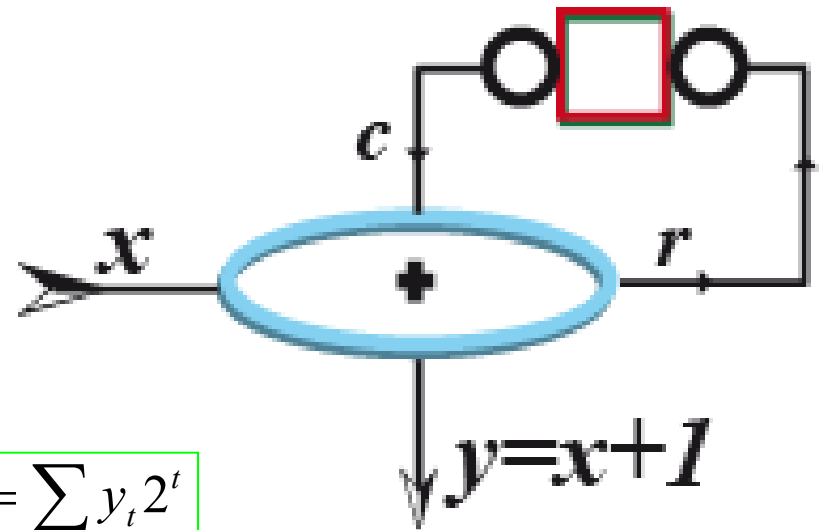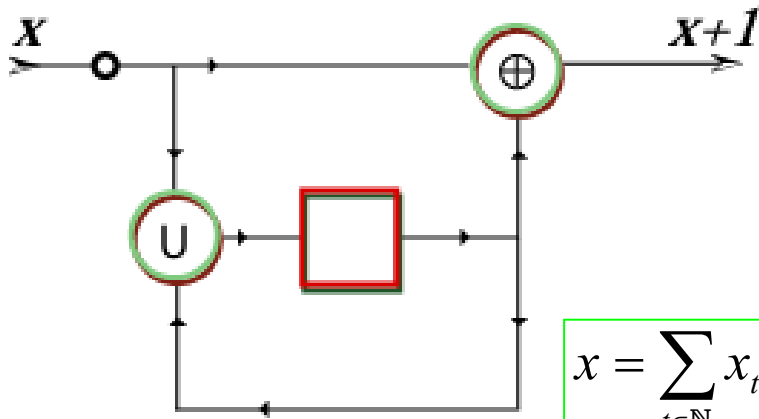

$$\begin{aligned}
 x &= \sum_{t \in \mathbb{N}} x_t 2^t & y &= \sum_{t \in \mathbb{N}} y_t 2^t \\
 c &= \sum_{t \in \mathbb{N}} c_t 2^t & r &= \sum_{t \in \mathbb{N}} r_t 2^t
 \end{aligned}$$







$$\begin{aligned}
 c &= 1 + 2r \\
 x + c &= y + 2r
 \end{aligned}$$

$$\begin{aligned}
 \forall t \in \mathbb{N}: \\
 c_0 &= 1 & c_{t+1} &= r_t \\
 x_t + c_t &= y_t + 2r_t
 \end{aligned}$$


→ $y = x + 1$

One & Two's Complement
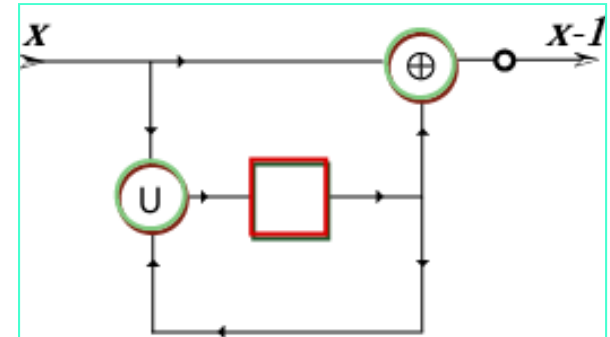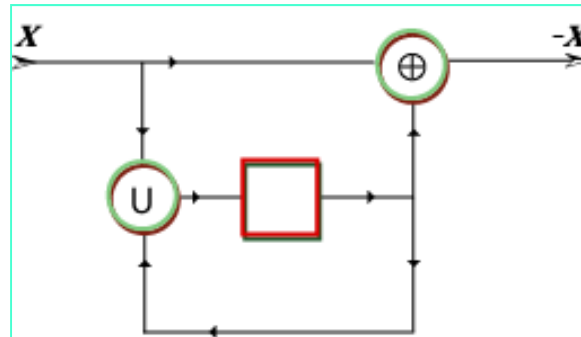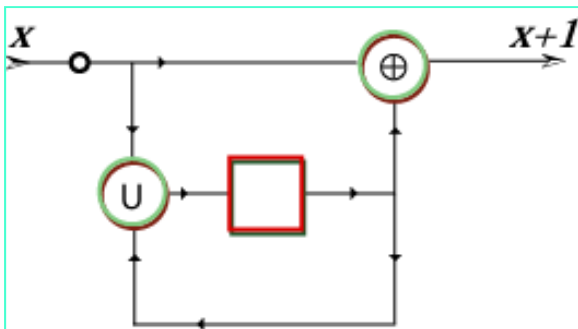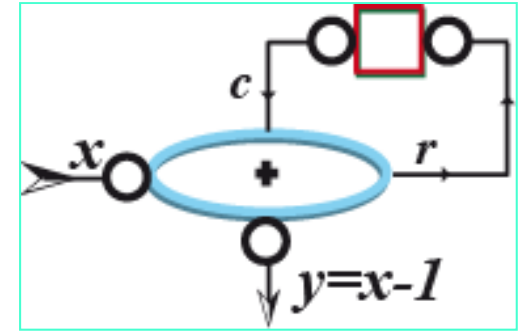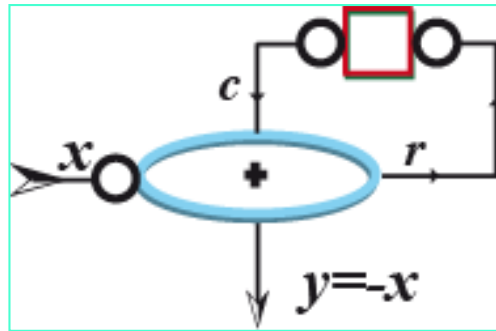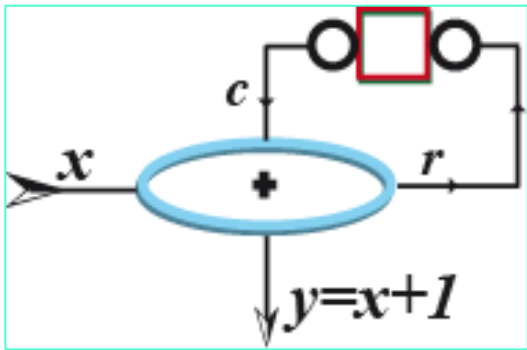
$$\begin{aligned}
 -1 &= x + \neg x \\
 -x &= 1 + \neg x \\
 x + 1 &= \neg \neg x \\
 x - 1 &= \neg \neg x
 \end{aligned}$$



Full Adder

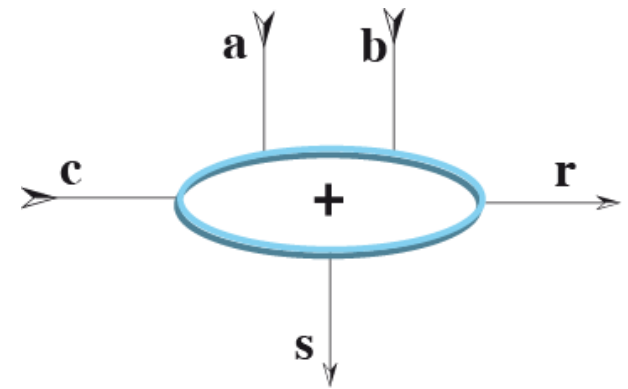


$$\text{fullAdd}(a,b,c) = (s,r)$$

$$\{ (p,g) = \text{halfAdd}(a,b)$$

$$(s,d) = \text{halfAdd}(c,g)$$


$$r = g \oplus d \}$$

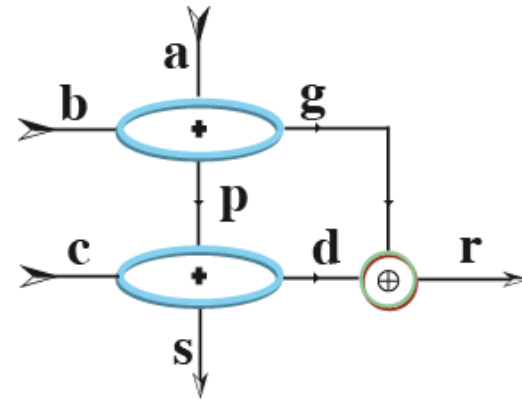

$$p = a \oplus b \quad g = a \cap b$$

$$s = c \oplus p \quad d = c \cap p$$

$$r = g \oplus d$$

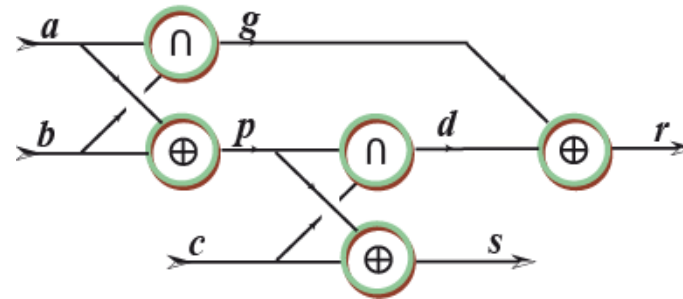


$$a + b = p + 2g$$

$$c + p = s + 2d$$

$$r = g + d$$

$$a + b + c = s + 2r$$

Parallel Adder

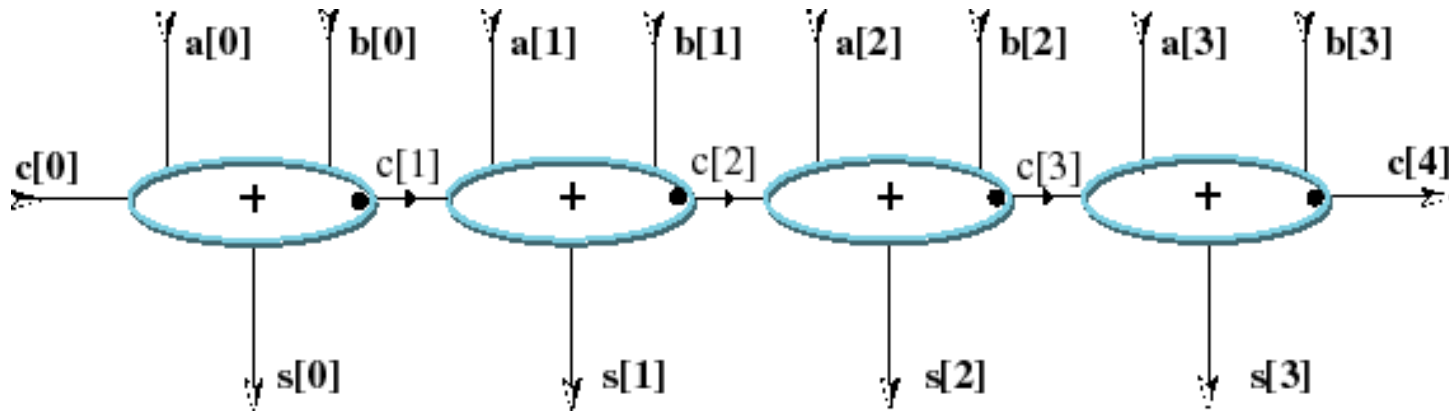


$$a_0 + b_0 + c_0 = s_0 + 2c_1$$

$$a_1 + b_1 + c_1 = s_1 + 2c_2$$


...

$$c_0 + \sum_{k < N} a_k 2^k + \sum_{k < N} b_k 2^k = \sum_{k < N} s_k 2^k + c_N 2^N$$

Serial Adder

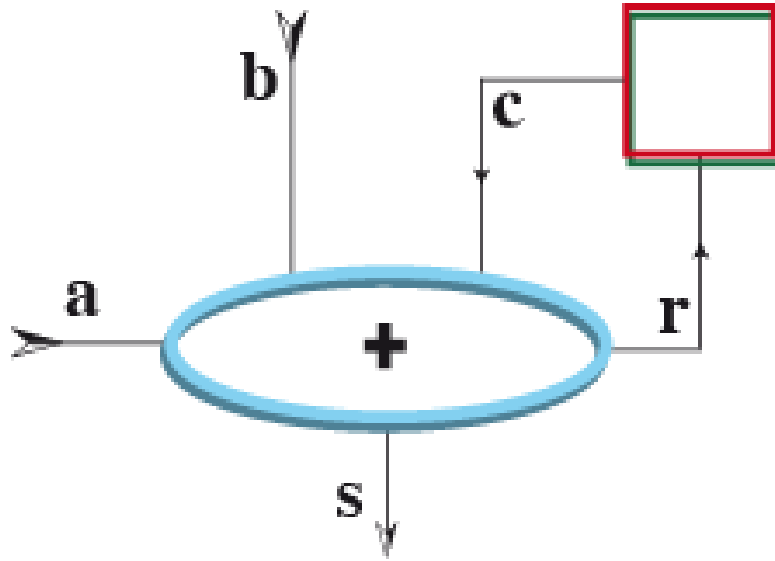

$$c = 2r$$
$$a + b + c = s + 2r$$

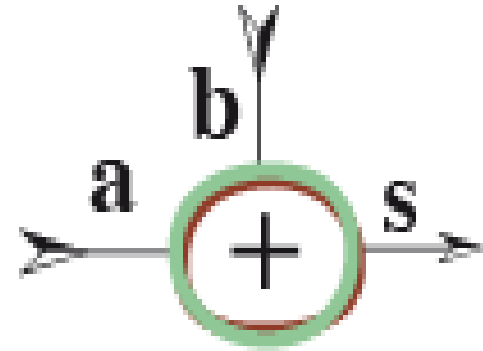

$$s = a + b$$

Beyond Addition

$$a = 2(x + 2a)$$

$$a = -\frac{2x}{3}$$

$$a = {}_2(01)^\infty \times x$$


$$b = x + a$$

$$b = \frac{x}{3}$$

$$\frac{1}{3} = {}_21(10)^\infty$$

$$y = b + 2b$$

$$y = x$$

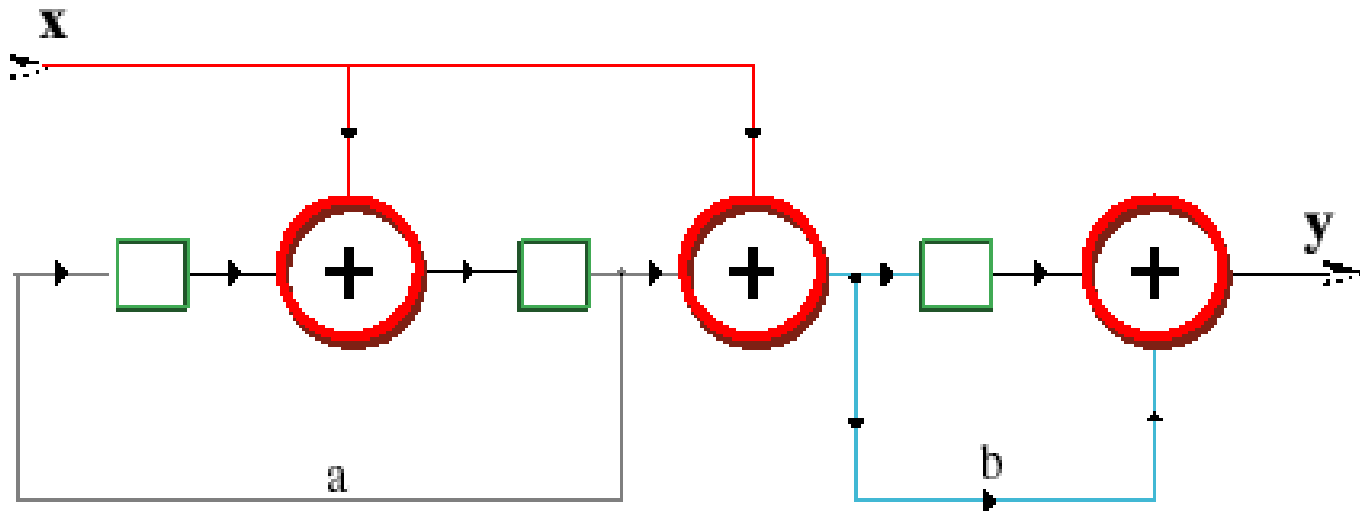

Large Hadron Collider



> 100 TB/s





9 km

Lake of Geneva






~ 100 GB/s

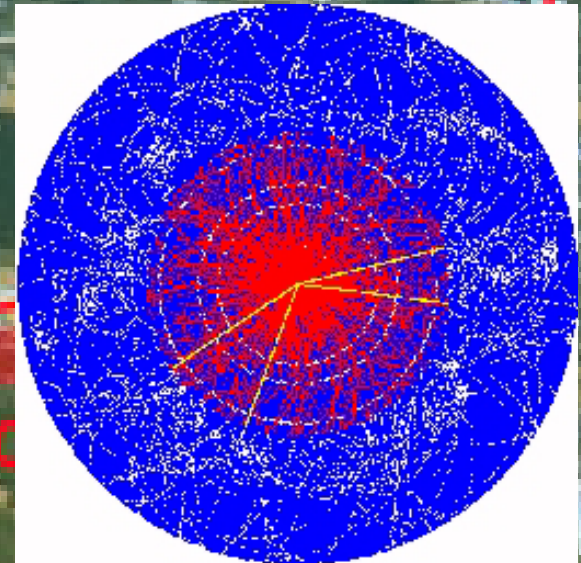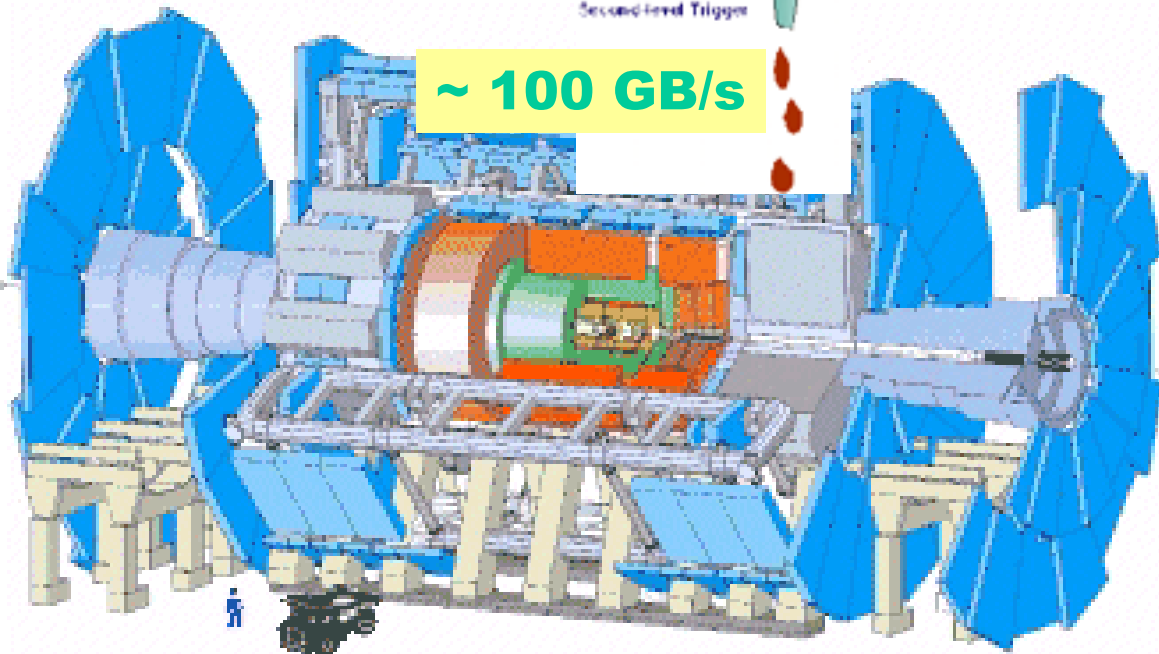


Transition Radiation Tracker

ATLAS Barrel Inner Detector
H. Aki

Region of interest

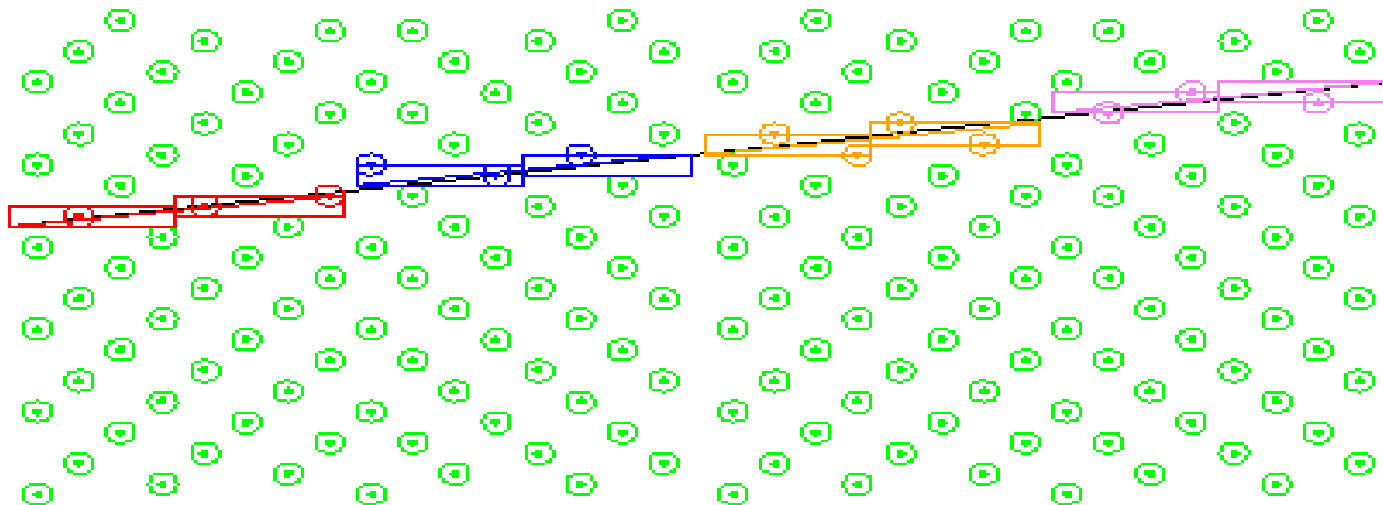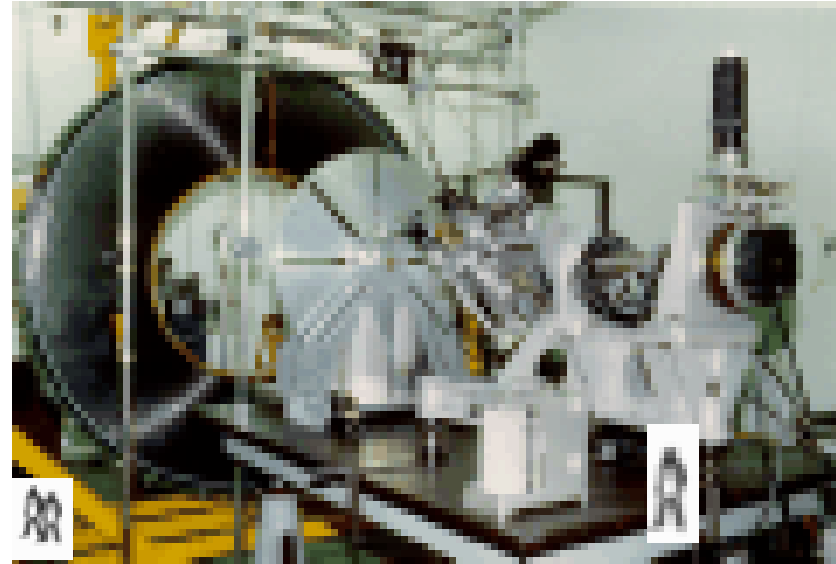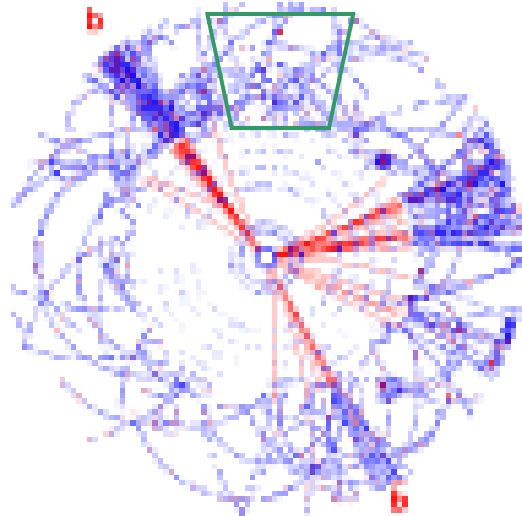

Linear Hough Transform

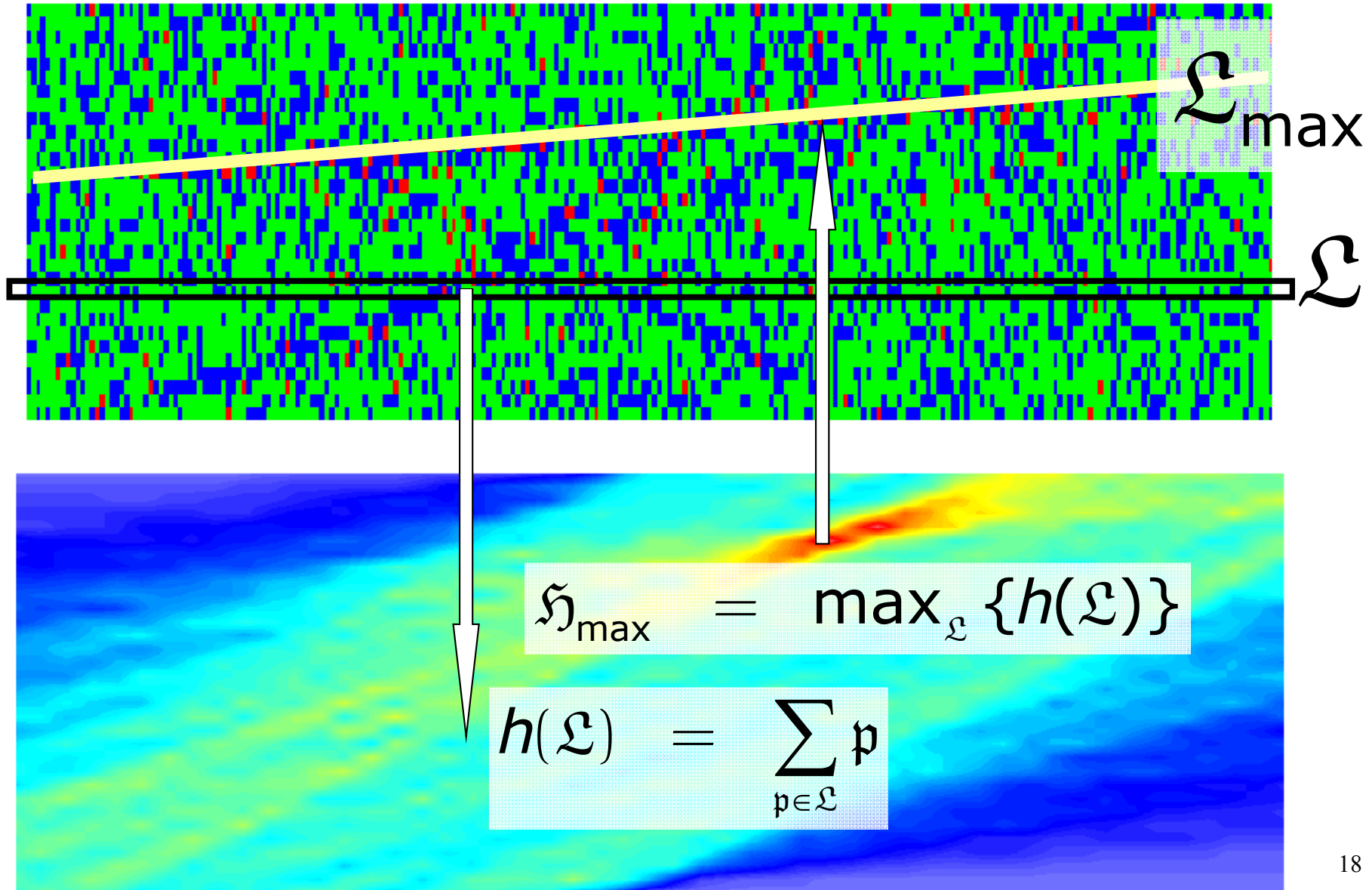

Input Receiver

FHT

Adders &


Line Delay

Network


Bit Reverse

Max Column

Max Rows

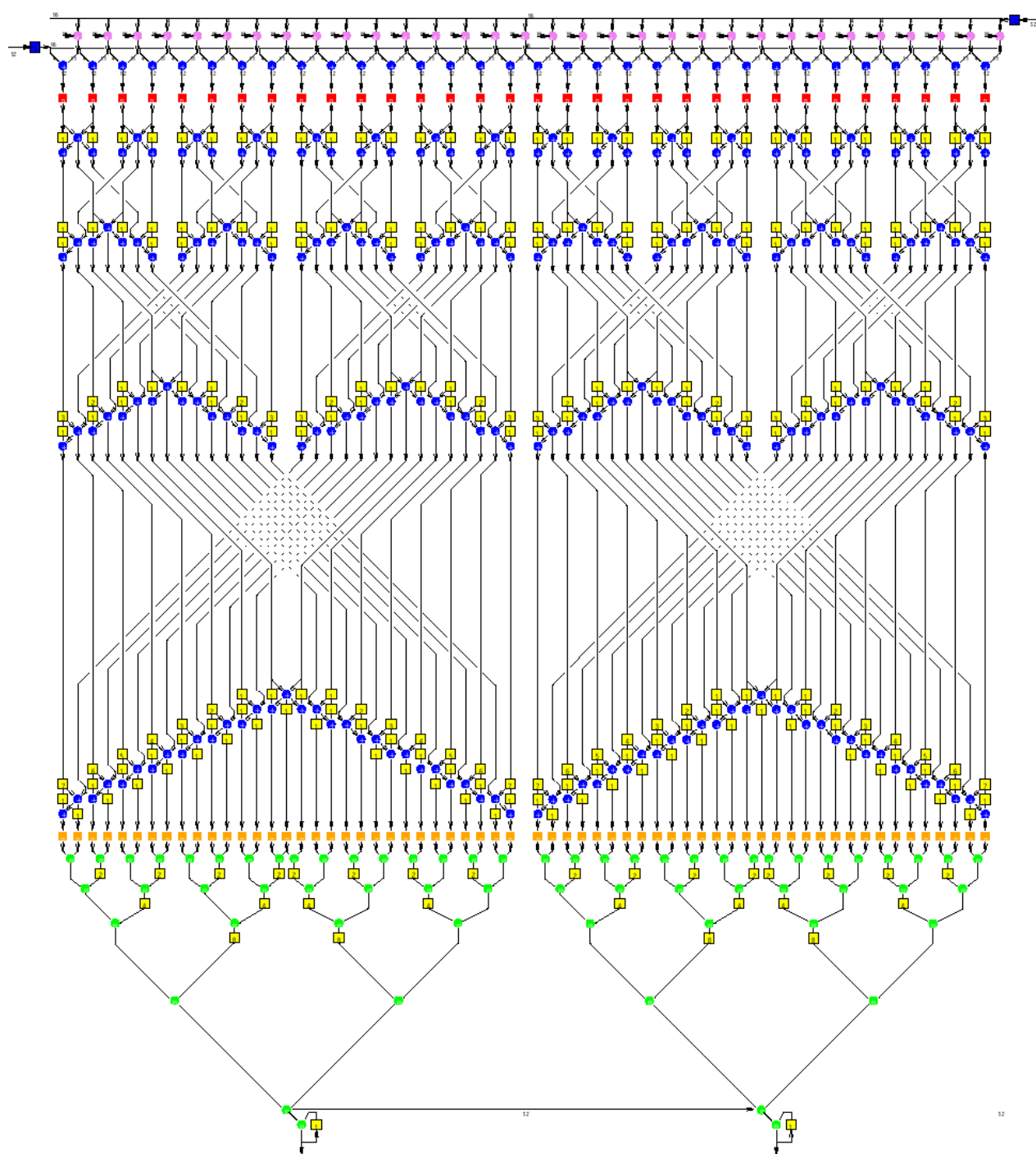

Trade Time For Space

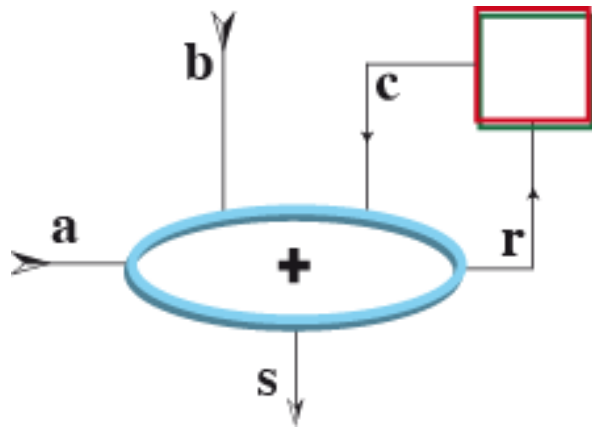


$$a = \sum a_k Z^k$$

$$Z=2 : 1b/cycle$$


$$a = \sum (a_0 + 2a_1) Z^k$$

$$Z=4 : 2b/cycle$$

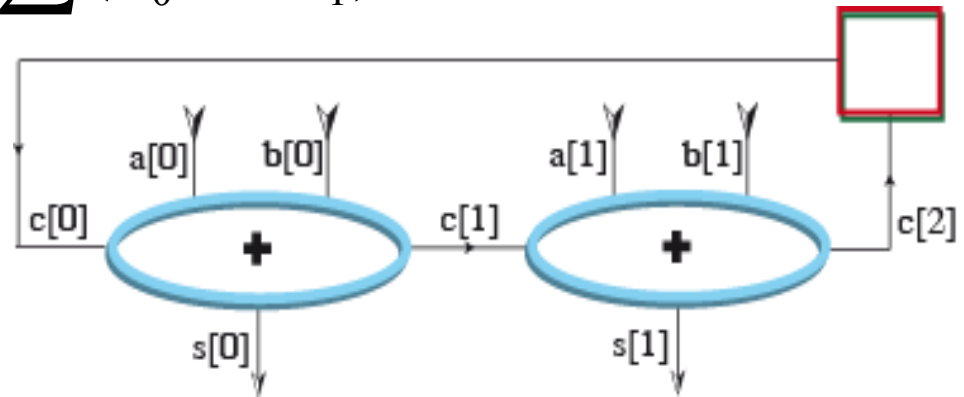

$$a = \sum a_{2k} 2^k + \sqrt{2} \sum a_{1+2k} 2^k \dots$$

$$Z=\sqrt{2} : 0.5b/cycle$$

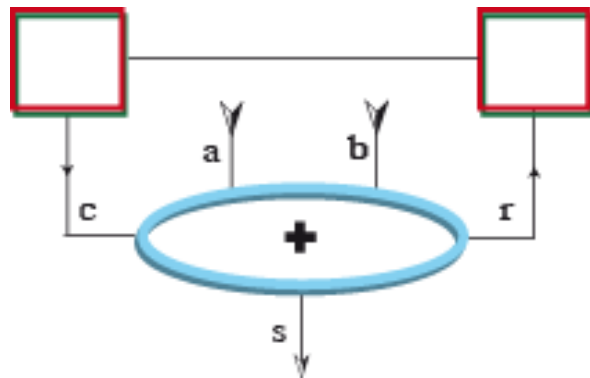

Energy is #1 design criteria for both hard & soft,
hence minimal computation at minimal speed!

Questions!